Jahangirnagar University
জাহাঙ্গীরনগর বিশ্ববিদ্যালয়

Department of Computer Science and Engineering

2nd Year 1st Semester (Hons)

Course Title: Digital Logic Design

Course Code: CSE-253

An Assignment on

1. 16 x 8 RAM using 8 x 4 Ram chips
2. Internal Structure of 16 x 4 RAM
3. 32 x 8 RAM using 8 x 4 Ram chips

Submitted To:

Nadia Afrin Ritu, B.Sc (JU), MSc. (JU)

Assistant Professor,

Department of Computer Science and Engineering,
Jahangirnagar University, Savar, Dhaka-1340.

Submitted By:

Name:	Murad Hossain Rohan
Roll:	338
Registration:	20230657073
Session:	2022-23
Exam Roll:	231041
Batch:	52

1. Draw the circuit diagram of a 16×8 RAM using 8×4 RAM chips.

$$\text{Necessary chips} = \frac{16 \times 8}{8 \times 4} = 4$$


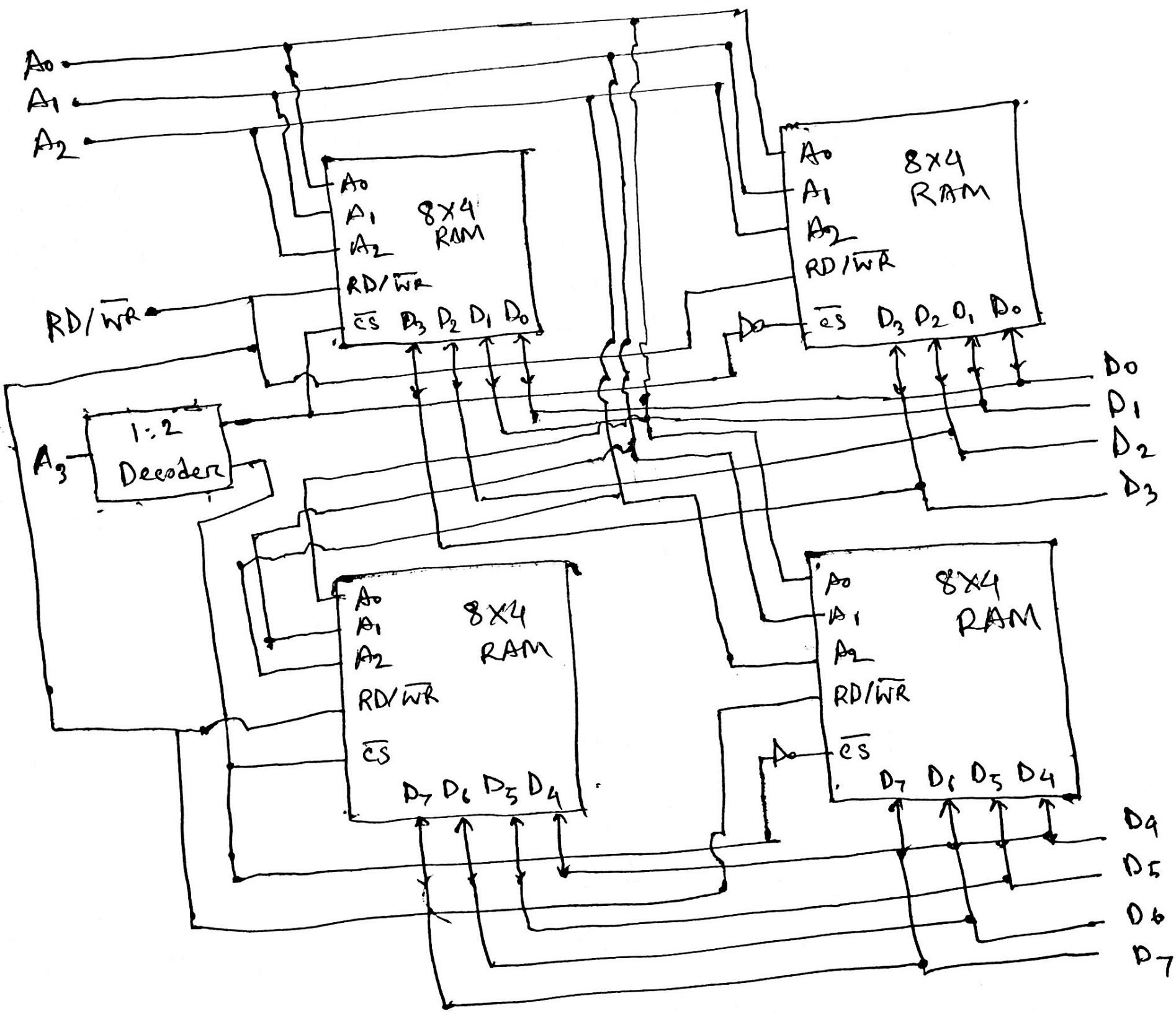


Fig: 16×8 RAM using 4 8×4 RAM chips

2. Draw The ~~internal~~ internal structure of

16×8 RAM

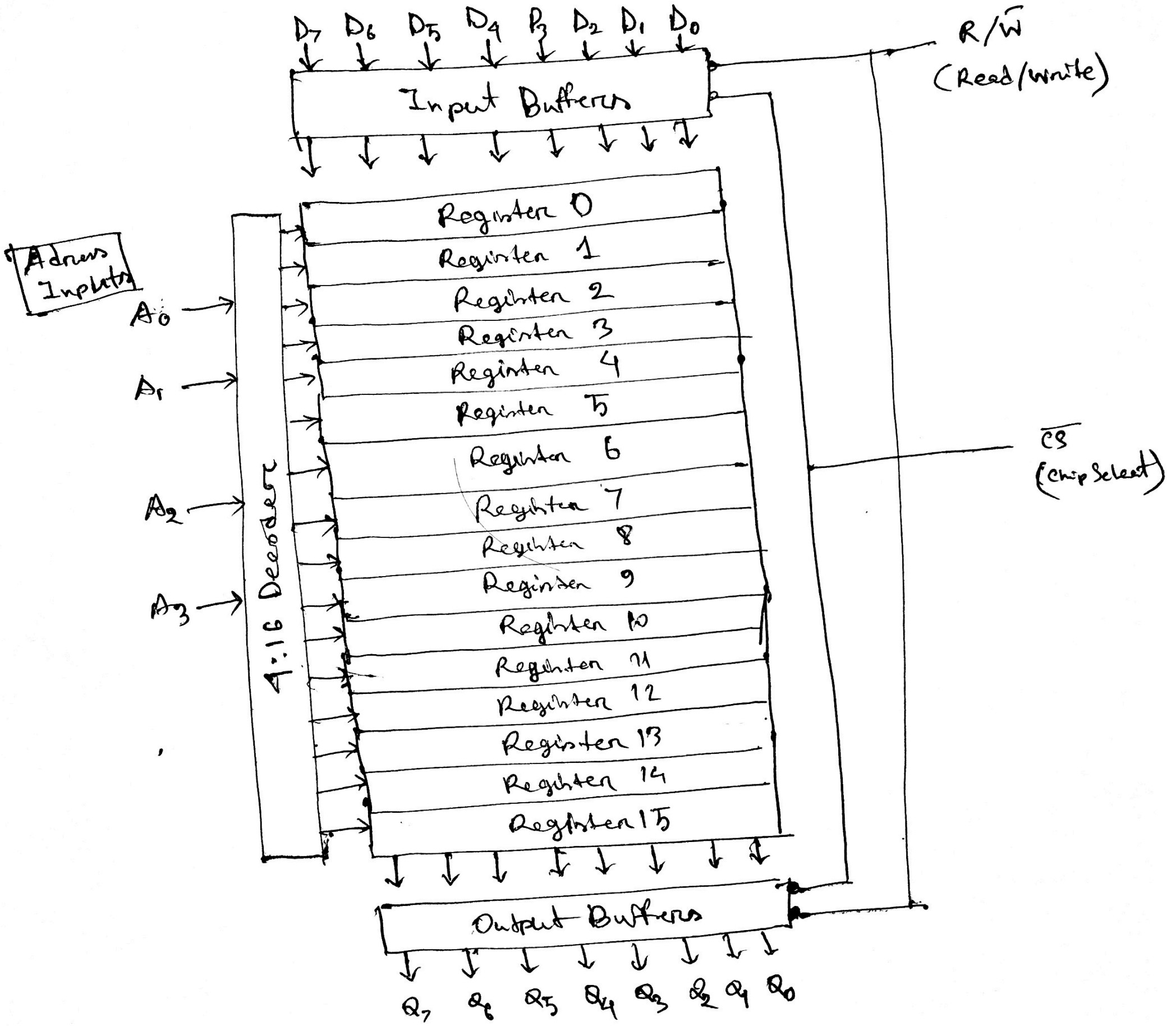

3. Draw the circuit diagram of a 32×8 RAM using 8×4 RAM chips.

Required chips = $\frac{32 \times 8}{8 \times 4}$ = 8 chips

